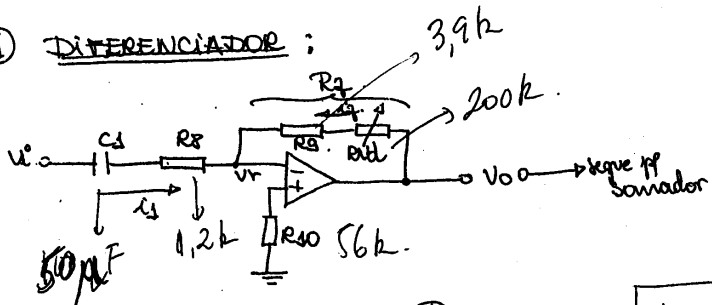


PID Analógico  
TORNEIRA ELÉTRICA


① DIFERENCIADOR :



$$X_C = \frac{1}{\omega C} = \frac{1}{f \omega C}$$

$$\frac{V_o}{V_i} = \frac{R_f}{R_i + \frac{1}{sC_i}} = \frac{R_f}{R_i C_i s + 1} \Rightarrow$$
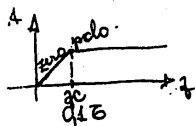
$$\frac{V_o}{V_i} = \frac{R_f C_i s}{R_i C_i s + 1}$$



(introduzindo polo pelo resistor  $R_i$  - filtra ruídos de alta frequência).

$$\frac{V_o}{V_i} = \frac{\tau_d s}{0.1 \tau_d s + 1}$$

Diferenciador


onde:  $\tau_d = R_f C_i \Rightarrow \tau_d = (R_g + R_{sd}) C_i$

- pf  $R_{sd} \max \Rightarrow \tau_d = 20,4 \text{ s} / 2$   $K_d = \frac{1}{\tau_d}$
- pf  $R_{sd} \min \Rightarrow \tau_d = 0,39 \text{ s} / 2$
- pf eliminar  $\tau_d$ , abrir "jump" na saída do circuito.

obs: sem o resistor  $R_i$ :


$$\frac{V_o}{V_i} = \frac{R_f}{\frac{1}{sC_i}} \Rightarrow \frac{V_o}{V_i} = \frac{R_f C_i s}{\tau_d}$$

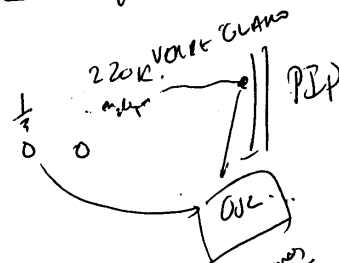$\rightarrow$  Introduz apenas um zero. Não é factível!!



Sempre filtrar

② INTEGRADOR:

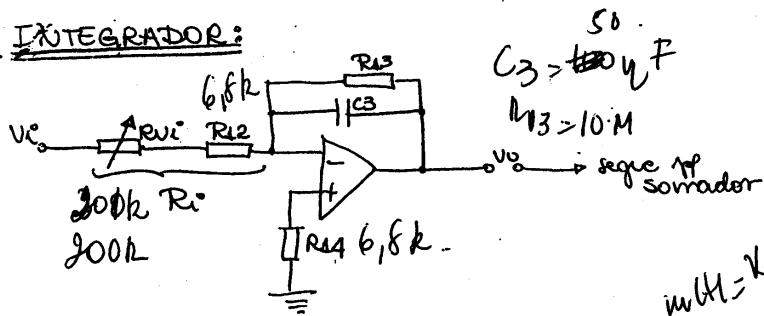

$w(t) = K_p [e^{st} + \frac{1}{T_i} \int e^{st} dt + e^{T_d s t}]$


$$\frac{V_o}{V_c} = \frac{R_{13} \frac{1}{sC_3}}{R_{13} + \frac{1}{sC_3}} = \frac{\frac{R_{13}}{sC_3}}{\frac{R_{13}C_3s + 1}{sC_3}} \Rightarrow \frac{V_o}{V_c} = \frac{R_{13}}{(R_{13}C_3s + 1)R_i}$$

$$\frac{V_o}{V_c} = \frac{1}{C_3 R_i s + \frac{R_i}{R_{13}}} \quad \text{O, pois } R_{13} = 10M\Omega \Rightarrow \frac{V_o}{V_c} = \frac{1}{R_i C_3 s + \frac{R_i}{R_{13}}}$$

onde:  $\tau_i = R_i C_3 \Rightarrow \tau_i = (R_{11} + R_{12}) \cdot C_3$

- p/  $R_{i\max} \Rightarrow \tau_i = 20,68s ; /2$
- p/  $R_{i\min} \Rightarrow \tau_i = 9,68s ; /2$
- p/ eliminar a ação integral, abrir "jump" na saída do circuito.

② PROPORCIONAL:

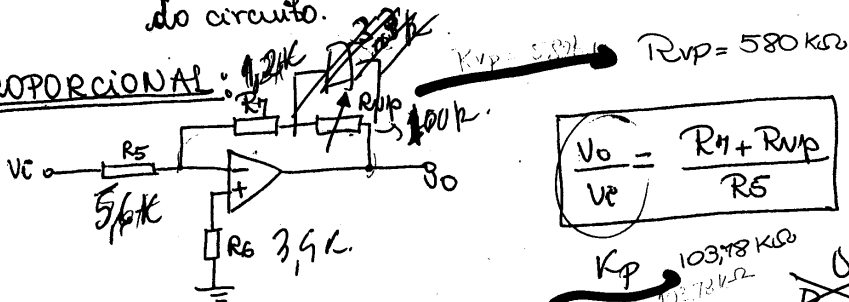

$$\frac{V_o}{V_c} = \frac{R_7 + R_{vp}}{R_5}$$

- $R_7 = 220 K\Omega$
- $R_{vp} = 220 K\Omega$
- $R_5 = 5,6 K$

- $K_p = 103,78 K\Omega$
- $K_{p\max} = 18,6$
- $K_{p\min} = 40$
- $R_{vp} = 31,2 K$
- $0,214 K\Omega$