
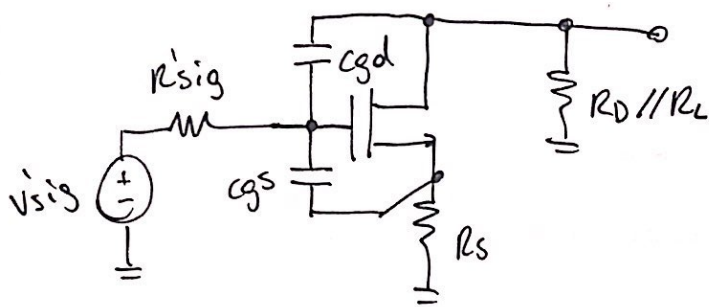


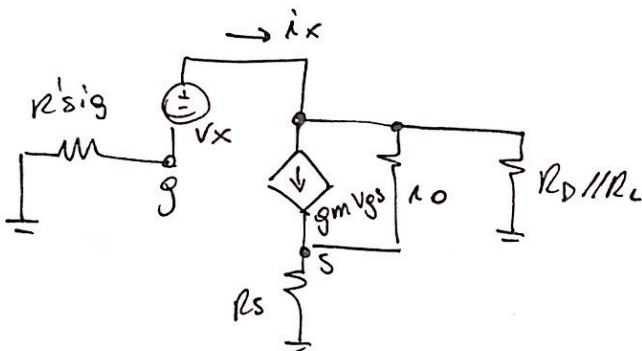- Nota de aula CEA → Análise WH de amplificador Common-Source com R_s .




→ Levantando R_{gd}




→ Modelando o transistor pelo modelo norton

→

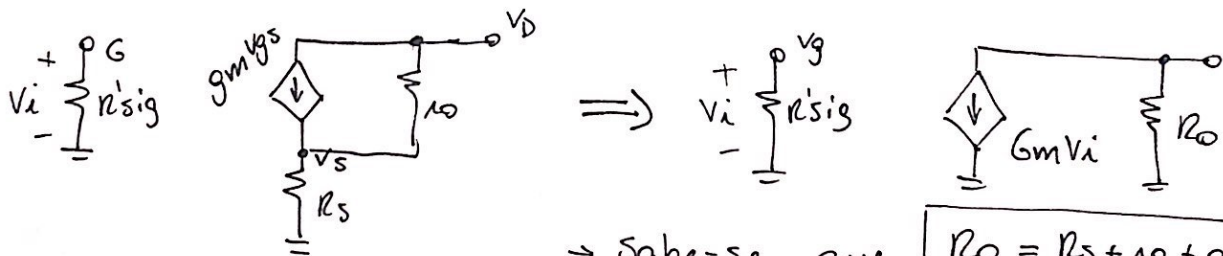

→ Sabe-se que $R_o = R_s + r_o + g_m R_s r_o$

→ cálculo de G_m

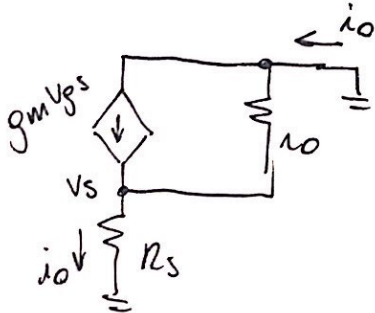

$$i_o = G_m v_i$$

→ sabe-se que $v_g = v_i$ e $v_s = i_o \cdot R_s$

logo, $v_{gs} = v_i - R_s i_o$



assim: $i_o = g_m v_{gs} + \left(\frac{-v_s}{r_o} \right)$

$$i_o = g_m v_i - g_m R_s i_o + \frac{R_s}{r_o} \cdot i_o$$

$$i_o \left(g_m R_s + \frac{R_s}{r_o} + 1 \right) = g_m v_i$$

$$G_m = \frac{g_m r_o}{r_o + R_s + g_m r_o R_s}$$

Assim, o circuito vira:

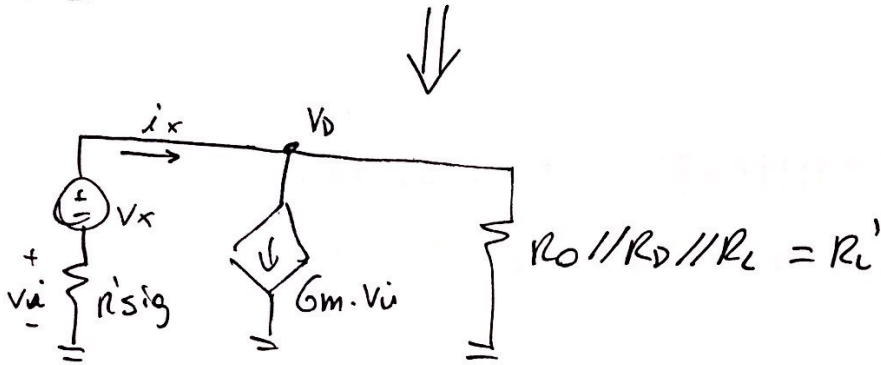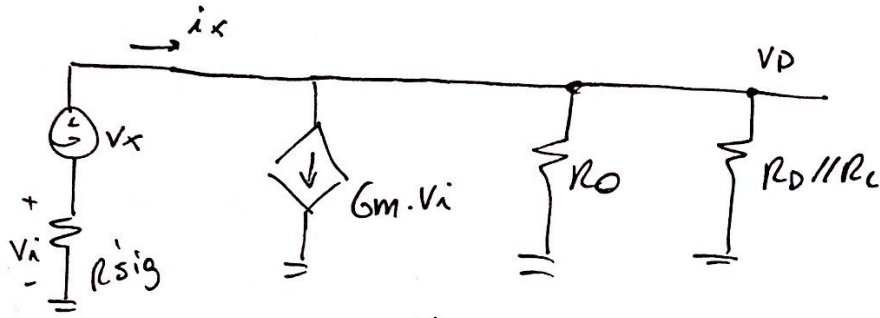


$$V_i = -i_x \cdot r'_{sig} \rightarrow V_D = V_x + V_i = V_x - r'_{sig} i_x$$

$$i_x = G_m \cdot V_i + \frac{V_D}{R_L'} \rightarrow i_x = -G_m r'_{sig} i_x + \frac{V_x}{R_L'} - \frac{r'_{sig}}{R_L'} \cdot i_x$$

$$i_x \left(1 + G_m r'_{sig} + \frac{r'_{sig}}{R_L'} \right) = \frac{V_x}{R_L'} \Rightarrow \boxed{\frac{V_x}{i_x} = R_{gd} = R_L' + G_m R_L' r'_{sig} + r'_{sig}}$$

→ Levantando Rgs

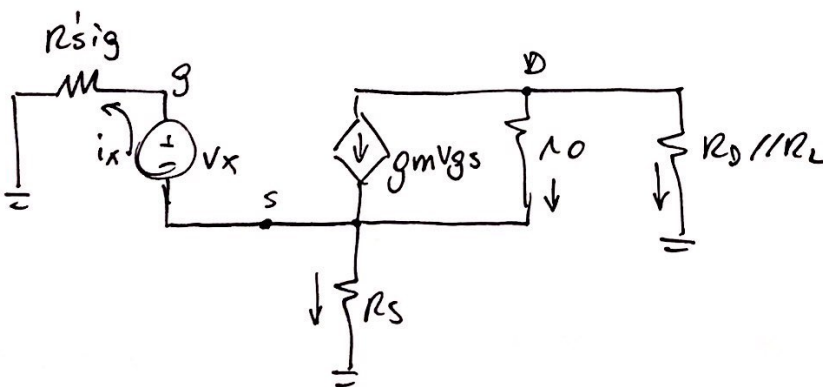

$$\begin{aligned} \rightarrow \text{No } S: \quad i_x + \frac{V_S}{R_S} &= g_m v_{gs} + \frac{V_D - V_S}{R_O} \\ \text{No } D: \quad g_m v_{gs} + \frac{V_D - V_S}{R_O} + \frac{V_D}{R_D // R_L} &= 0 \end{aligned} \quad \left| \begin{array}{l} v_{gs} = V_x \\ v_g = r'_{sig} \cdot i_x \\ v_s = r'_{sig} \cdot i_x - V_x \end{array} \right.$$

→ Assim,

$$\text{Nó S: } i_x + v_s \left(\frac{1}{R_s} + \frac{1}{r_o} \right) - g_m v_x = \frac{v_D}{r_o}$$

$$v_D = r_o i_x + v_s \left(1 + \frac{r_o}{R_s} \right) - g_m r_o v_x$$

$$\text{Nó D: } g_m v_x + v_D \left(\frac{1}{r_o} + \frac{1}{R_D // R_L} \right) - \frac{v_s}{r_o}$$

$$g_m r_o v_x + v_D \left(1 + \frac{r_o}{R_D // R_L} \right) - v_s = 0$$

→ Substituindo v_D na equação acima

$$g_m r_o v_x - v_s + \left(1 + \frac{r_o}{R_D // R_L} \right) \left[r_o i_x + \left(1 + \frac{r_o}{R_s} \right) v_s - g_m r_o v_x \right] = 0$$

$$r_o \left(1 + \frac{r_o}{R_D // R_L} \right) i_x + \left(g_m r_o - g_m r_o + \frac{g_m r_o^2}{R_D // R_L} \right) v_x + \left[-1 + \left(1 + \frac{r_o}{R_D // R_L} \right) \left(1 + \frac{r_o}{R_s} \right) \right] v_s = 0$$

$$\frac{r_o (R_D // R_L) + r_o^2}{R_D // R_L} \cdot i_x - \frac{g_m r_o^2}{R_D // R_L} v_x + \frac{(R_D // R_L) r_o + r_o R_s + r_o^2}{R_s R_D // R_L} \cdot v_s = 0$$

$$(r_o^2 R_s + r_o R_s (R_D // R_L)) i_x - g_m r_o^2 R_s v_x + [(R_D // R_L) r_o + r_o R_s + r_o^2] v_s = 0$$

→ Substituindo o valor de v_s :

$$0 = [r_o^2 R_s + r_o R_s (R_D // R_L)] i_x - g_m r_o^2 R_s v_x$$

$$+ [(R_D // R_L) r_o + r_o R_s + r_o^2] r'_{sig} i_x - [(R_D // R_L) r_o + r_o R_s + r_o^2] v_x$$

$$v_x (g_m R_s r_o^2 + r_o^2 + (R_D // R_L) r_o + r_o R_s) = \left[r_o^2 R_s + r_o R_s (R_D // R_L) + (R_D // R_L) r_o r'_{sig} + r_o R_s r'_{sig} + r_o^2 r'_{sig} \right] i_x$$

$$\frac{v_x}{i_x} = R_{gs} = \frac{r_o^2 R_s + r_o R_s (R_D // R_L) + (R_D // R_L) r_o r'_{sig} + r_o R_s r'_{sig} + r_o^2 r'_{sig}}{r_o R_s + r_o^2 + (R_D // R_L) r_o + g_m R_s r_o^2}$$

$$= \frac{(R_D // R_L + r_o) (r'_{sig} + R_s) + r'_{sig} R_s}{(R_D // R_L + r_o) + (g_m R_s r_o + R_s)}$$

$$R_{gs} = \frac{r'_{sig} + R_s + r'_{sig} R_s / (R_D // R_L + r_o)}{1 + (g_m R_s r_o + R_s) / (R_D // R_L + r_o)}$$

$$W_H = \frac{1}{C_{gs} R_{gs} + C_{gd} R_{gd}}$$