
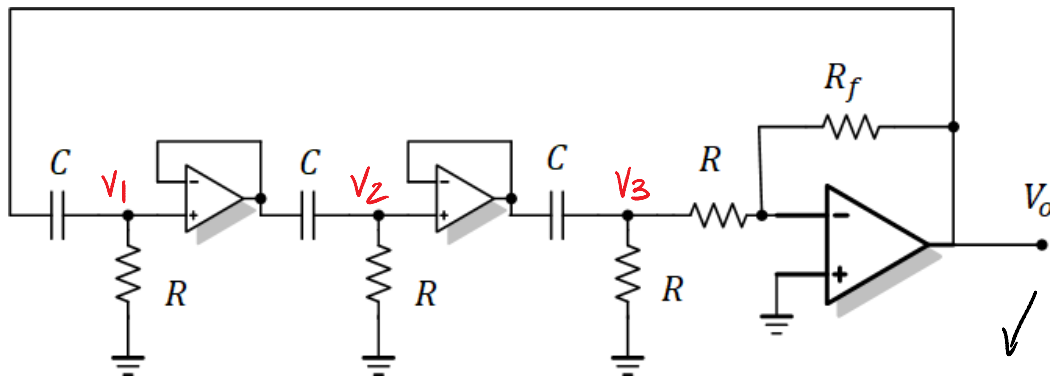


Resolução Ex 10 - CEA

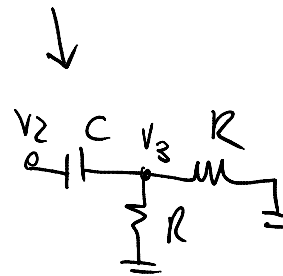

$$a) \quad V_1 = \frac{R V_0}{R + 1/sC} = \frac{sCR}{sCR + 1} V_0$$

$$V_2 = \frac{sCR}{sCR + 1} \cdot V_1$$



$$V_3 = V_2 \cdot \frac{R/2}{1/sC + R/2} = \frac{sCR}{sCR + 2}$$

$$V_0 = -\frac{Rf}{R} \cdot V_3$$

• Assim:
$$A\beta = \frac{V_1}{V_0} \cdot \frac{V_2}{V_1} \cdot \frac{V_3}{V_2} \cdot \frac{V_0}{V_3} = -\frac{Rf}{R} \frac{(sCR)^3}{(sCR + 1)^2 (sCR + 2)}$$

$$\rightarrow \log A\beta = -\frac{Rf}{R} \frac{(sCR)^3}{(sCR)^3 + 4(sCR)^2 + 5sCR + 2}$$

fazendo $s = j\omega \rightarrow L(j\omega) = A\beta(j\omega) = \frac{Rf/R \cdot j\omega^3 C^3 R^3}{-j(\omega CR)^3 - 4(\omega CR)^2 + j5\omega CR + 2}$

$$L(j\omega) = \frac{j \frac{Rf}{R} (\omega CR)^3}{(2 - 4(\omega CR)^2) + j(5\omega CR - (\omega CR)^3)} \times \frac{j}{j}$$

$$L(j\omega) = \frac{-\frac{R_f}{R} (\omega CR)^3}{-[5\omega CR - (\omega CR)^3] + j[2 - 4(\omega CR)^2]}$$

• P/ $L(j\omega_0) = 1$, tem-se que

• $2 - 4\omega_0^2 C^2 R^2 = 0 \Rightarrow \boxed{\omega_0 = \frac{1}{CR\sqrt{2}}}$

• $\frac{R_f}{R} \omega_0^3 C^3 R^3 = 5\omega_0 CR - \omega_0^3 C^3 R^3$

$$\frac{R_f}{R} \omega_0^2 C^2 R^2 = 5 - \omega_0^2 C^2 R^2$$

$$\frac{R_f}{R} \cdot \frac{1}{2} = 5 - \frac{1}{2} \Rightarrow \boxed{R_f = 9R}$$


b) P/ $\omega_0 = 2\pi \cdot 10k \text{ Hz}$

• Assumindo $R = 10k \Omega$

$$R_f > 90k \Omega$$

$$C = \frac{1}{R \cdot \omega_0 \sqrt{2}} = 1,12 \text{ nF}$$

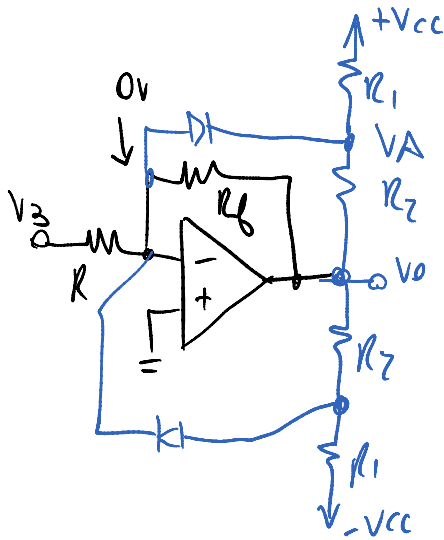c) Projete um limitador p/ $\hat{V}_o = 8V$, sendo $V_{CC} = 15V$.



$$V_A = \frac{15R_2}{R_1 + R_2} + \frac{V_o R_1}{R_1 + R_2}$$

Quando $\hat{V}_o = -8V \rightarrow V_A = -0,7V$

$$-0,7(R_1 + R_2) = 15R_2 - 8R_1$$

$$15,7R_2 = 7,3R_1$$

$$\frac{R_2}{R_1} = 0,465 \quad \left. \begin{array}{l} \rightarrow R_1 = 10k\Omega \\ \rightarrow R_2 = 4,65k\Omega \end{array} \right\}$$