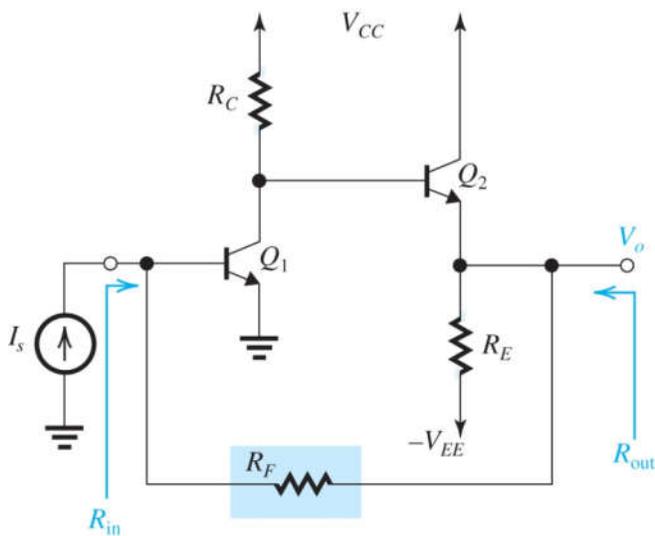


Resolução Exercício 9 - CEA




$$\rightarrow V_{CC} = V_{EE} = 5V;$$

$$R_C = R_E = R_F = 10k\Omega$$

$$\beta = 100$$

a) Realimentação Paralelo - Paralelo

b) Definir a polarização:

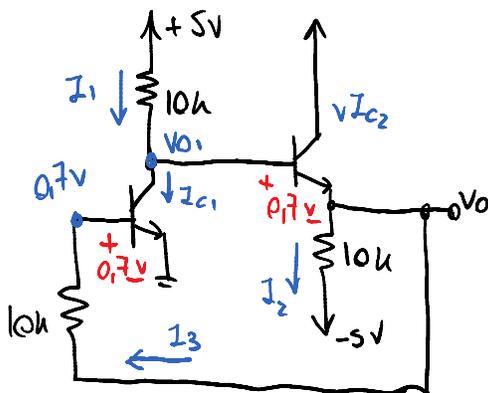

$$\cdot V_{01} = V_0 + 0,7V \quad ; \quad I_3 = I_{B1} = \frac{I_{C1}}{\beta}$$

$$I_{C1} = I_1 - I_{B2}$$

$$I_{E2} = I_2 + I_3$$

$$\rightarrow I_1 = \frac{5 - V_0 - 0,7}{10k}$$

$$I_2 = \frac{V_0 + 5}{10k} \quad ; \quad I_3 = \frac{V_0 - 0,7}{10k}$$

→ Assim,

$$\beta I_3 = I_1 - I_{E2}/\beta$$

$$\beta \left(\frac{V_0 - 0,7}{10k} \right) = \frac{4,3 - V_0}{10k} - \frac{V_0 + 5 + V_0 - 0,7}{\beta \cdot 10k}$$

$$\beta^2 (V_0 - 0,7) = \beta (4,3 - V_0) - 2V_0 - 4,3$$

$$V_0 (\beta^2 + \beta + 2) = 4,3\beta - 4,3 + 7000$$

$$\boxed{V_0 = 0,735V}$$

$$I_1 = 356,5 \mu A$$



$$I_2 = 573,5 \mu A$$

$$I_3 = 3,5 \mu A$$

$$\boxed{I_{C1} = 350,7 \mu A}$$

$$\boxed{I_{C2} = 571,3 \mu A}$$

c) Calcular o ganho de realimentação

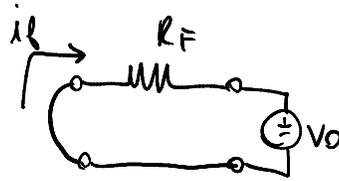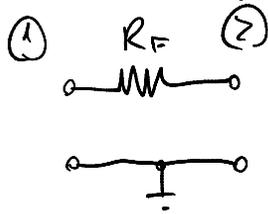

$$\beta = \frac{i_f}{V_O} = -\frac{1}{R_F}$$

$$\beta = -\frac{1}{10k} = -0,1 \text{ mA/V}$$


$$R_{11} = R_F$$

$$R_{22} = R_F$$

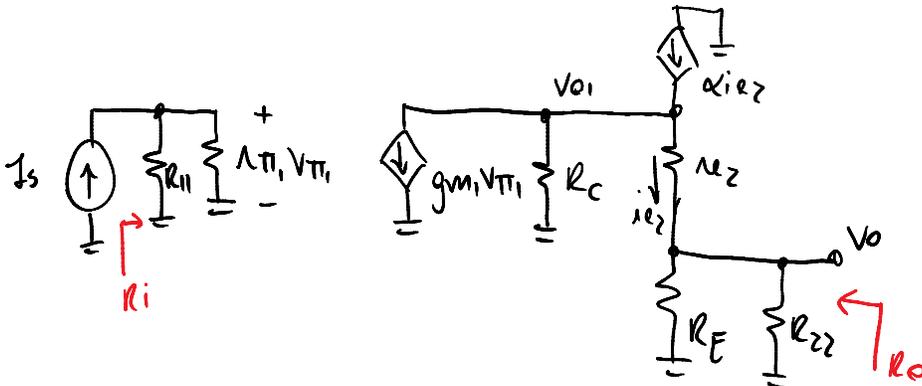d) Calcule o ganho A

$$\rightarrow \Delta = \frac{V_O}{i_S} ; \quad r_{\pi 1} = 7,13 \text{ k}\Omega \quad r_{e2} = 43,33 \Omega ; \quad V_A \text{ não foi informado, logo } r_{o1} = r_{o2} \rightarrow \infty$$

$$g_{m1} = 14 \text{ mA/V} \quad \alpha = 0,99$$



$$\rightarrow v_{\pi 1} = R_{11} // r_{\pi 1} \cdot i_S = 4,162 \text{ kV/A} \cdot i_S$$

$$v_{o1} = -g_{m1} \cdot v_{\pi 1} \cdot \left(R_C // \left(r_{e2} + R_E // R_{22} \right) (\beta + 1) \right) = -137,3 v_{\pi 1}$$

$$V_O = v_{o1} \cdot \frac{R_E // R_{22}}{r_{e2} + R_E // R_{22}} = 0,9914 \cdot v_{o1}$$

$$\rightarrow \text{logo, } \boxed{\frac{V_O}{i_S} = -566,53 \text{ kV/A}}$$

e) Calcular A_f , R_{in} e R_{out}

$$A\beta = -566,53 \text{ kV/A} \cdot -0,1 \text{ mA/V} = +56,65$$

$$A_f = \frac{A}{1+A\beta} = -9,83 \text{ kV/A}$$

$$R_i = R_{11} // R_{12} = 4,162 \text{ k}\Omega$$

$$R_o = R_E // R_{22} // \left(R_2 + \frac{R_C}{\beta+1} \right) = 138,4 \Omega$$

$$R_{if} = R_{in} = \frac{R_i}{1+A\beta} = 72,2 \Omega$$

obs : $R_s = \infty$

$$R_{out} = R_{of} = \frac{R_o}{1+A\beta} = 2,4 \Omega$$

obs : $R_L = \infty$